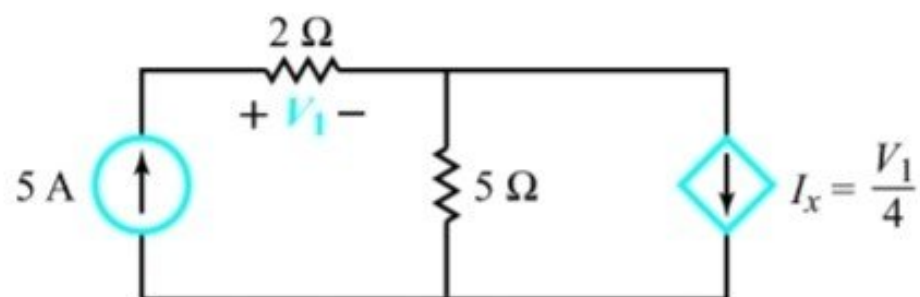


**Exercise 1-9** Find  $I_x$  from the diagram in Fig. E1-9.




**Figure E1-9**

**Solution:**

$$V_1 = 5 \times 2 = 10 \text{ V}$$

$$I_x = \frac{V_1}{4} = 2.5 \text{ A.}$$

**Exercise 2-4** If  $I_1 = 3$  A in Fig. E2-4, what is  $I_2$ ?

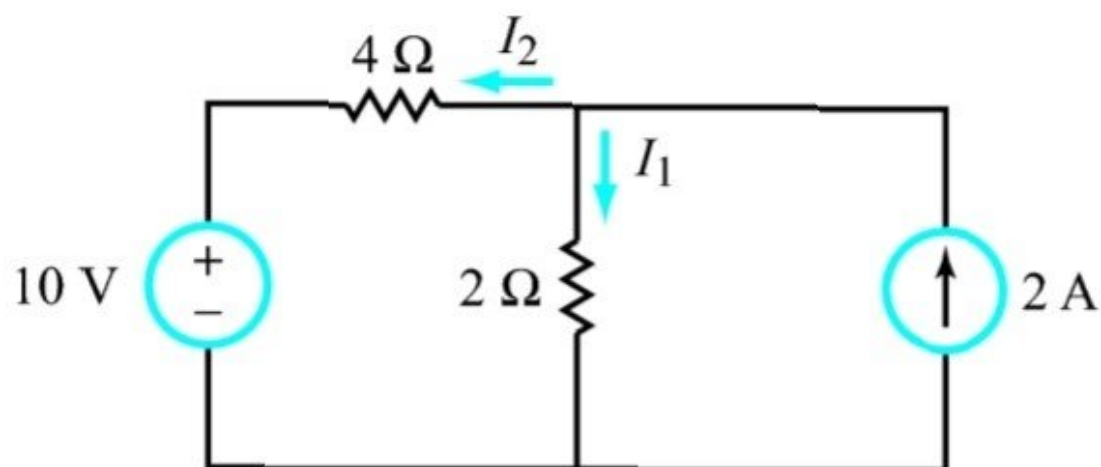

**Figure E2-4**


**Solution:** KCL at the top center node requires that

$$I_1 + I_2 - 2 \text{ A} = 0.$$

Hence,

$$I_2 = 2 - I_1 = 2 - 3 = -1 \text{ A}.$$

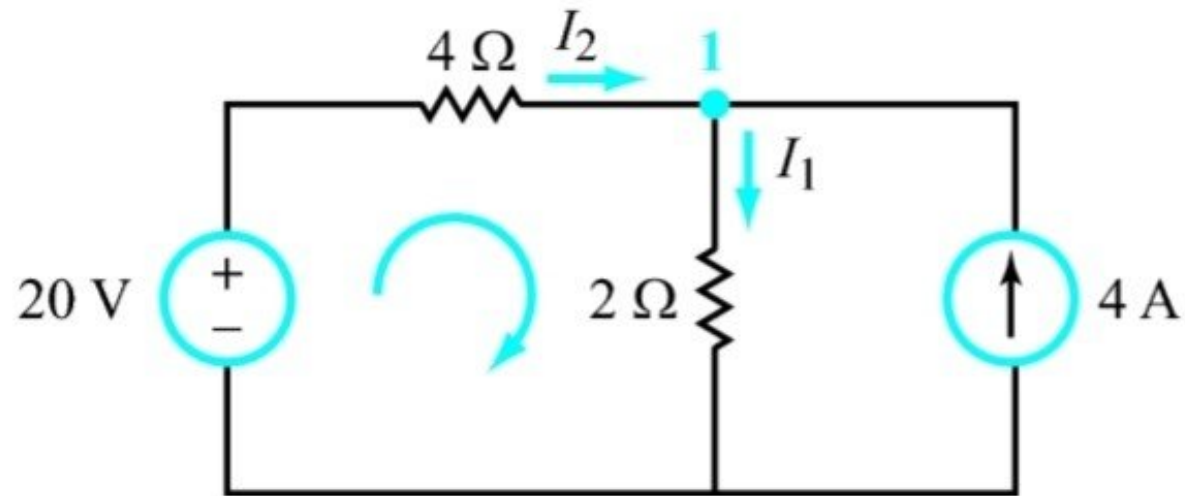**Exercise 2-5** Apply KCL and KVL to find  $I_1$  and  $I_2$  in Fig. E2-5.



**Solution:** KCL at node 1 requires that

$$I_1 = I_2 + 4.$$

Also, KVL for the left loop is

$$-20 + 4I_2 + 2I_1 = 0.$$


Simultaneous solution leads to

$$I_1 = 6 \text{ A}, \quad I_2 = 2 \text{ A}.$$



**Exercise 2-6** Determine  $I_x$  in the circuit of Fig. E2-6.

**Solution:**

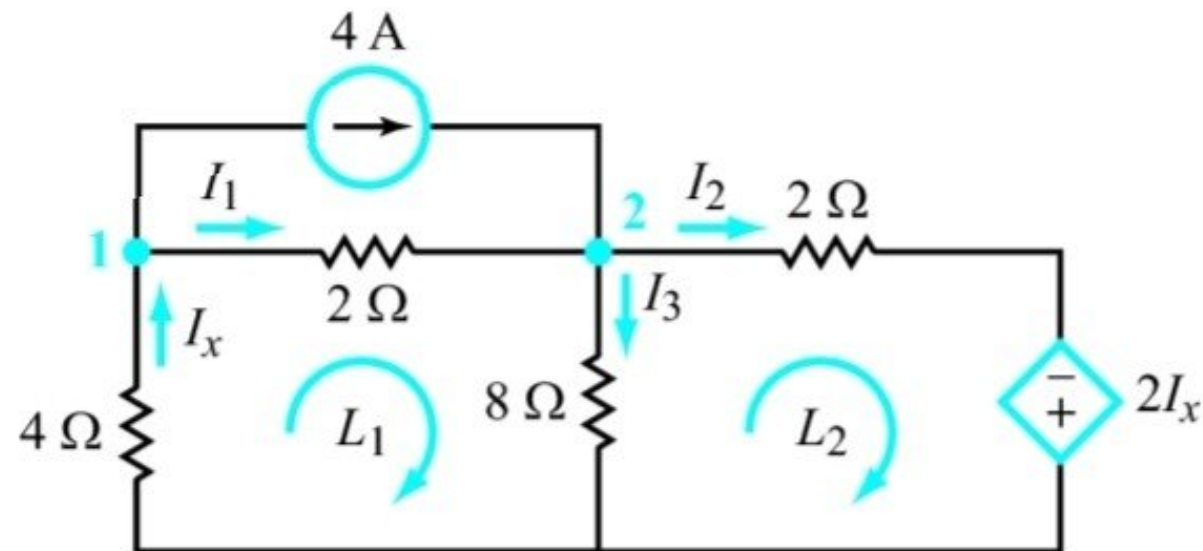

$$\text{KCL @ node 1: } I_x = I_1 + 4$$

$$\text{KCL @ node 2: } I_1 + 4 = I_2 + I_3$$

$$\text{KVL Loop 1: } 4I_x + 2I_1 + 8I_3 = 0$$

$$\text{KVL Loop 2: } -8I_3 + 2I_2 - 2I_x = 0$$

We have four equations with four unknowns. Simultaneous solution leads to

$$I_x = 1.33.$$

**Exercise 2-7** Apply resistance combining to simplify the circuit of Fig. E2-7 so as to find  $I$ . All resistor values are in ohms.



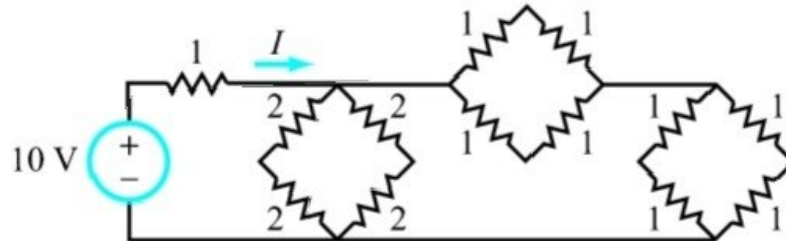


Figure E2-7

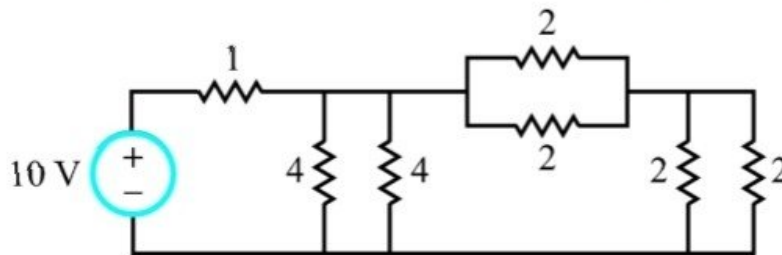**Solution:** Combining all resistors that are in series will result in the following circuit:



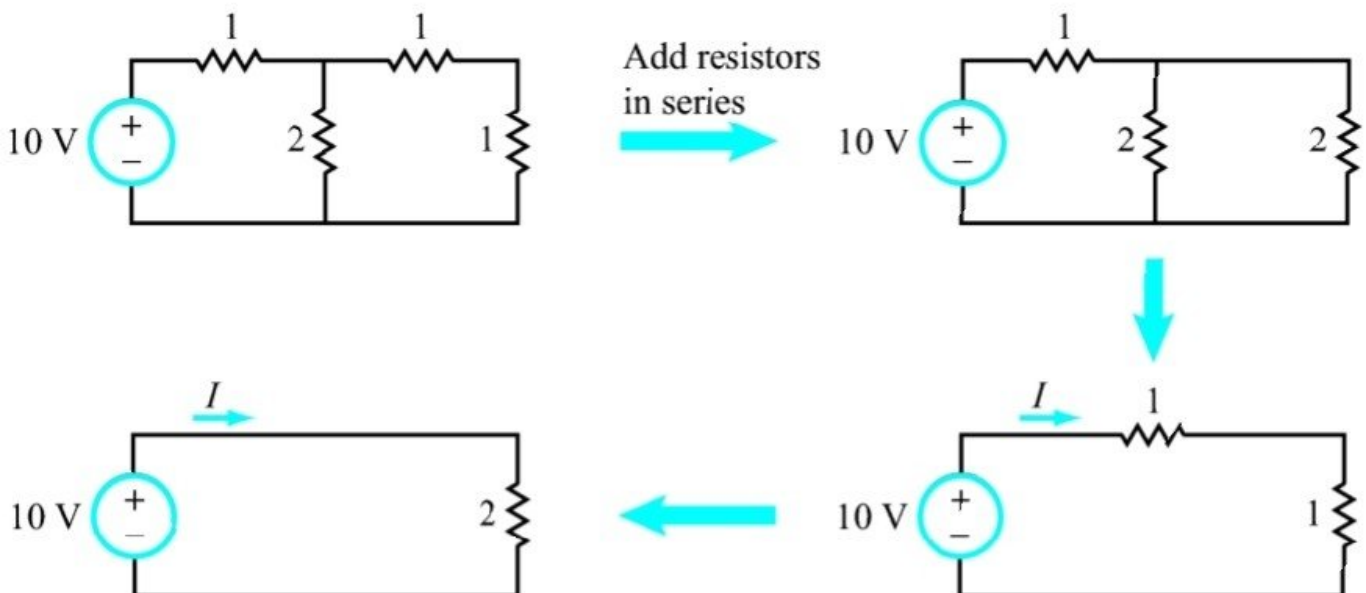Combining all resistors that are in parallel will result in:



$$I = \frac{10 \text{ V}}{2 \Omega} = 5 \text{ A.}$$

**Exercise 2-8** Apply source transformation to the circuit in Fig. E2-8 to find  $I$ .



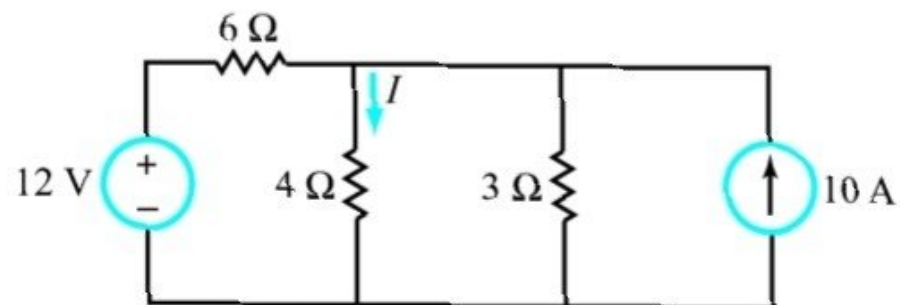


Figure E2-8

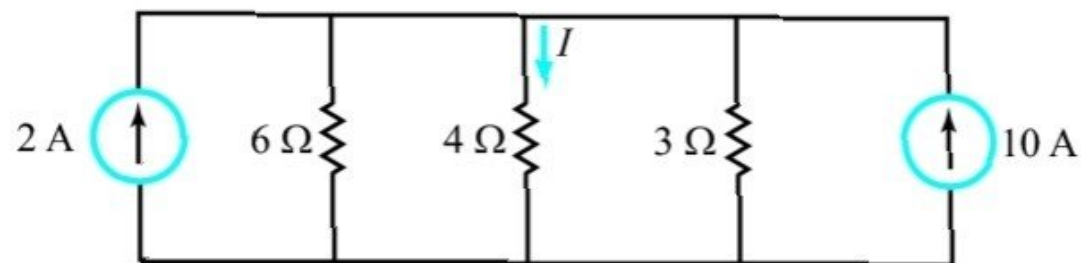**Solution:** Apply source transformation to the 12-V source and 6-Ω resistor:




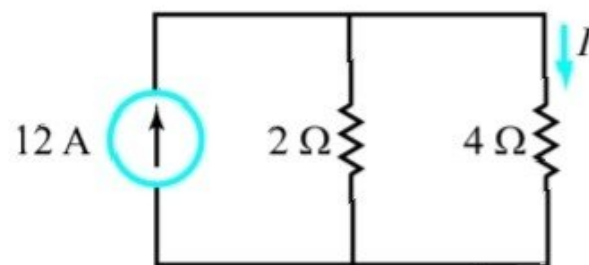
Combine current sources and combine 3-Ω and 6-Ω resistors, while leaving 4-Ω alone



Current division gives

$$I = \frac{12 \times 2}{2 + 4} = 4 \text{ A.}$$


**Exercise 2-9** For each of the circuits shown in Fig. E2-9, determine the equivalent resistance between terminals  $(a, b)$ .

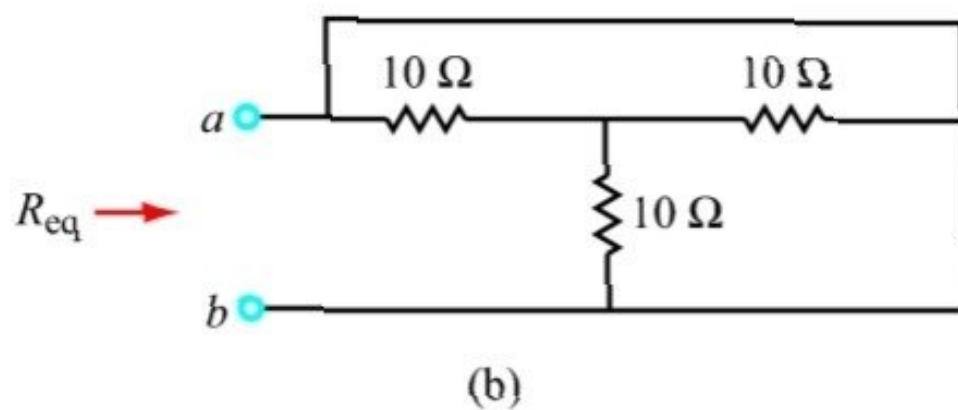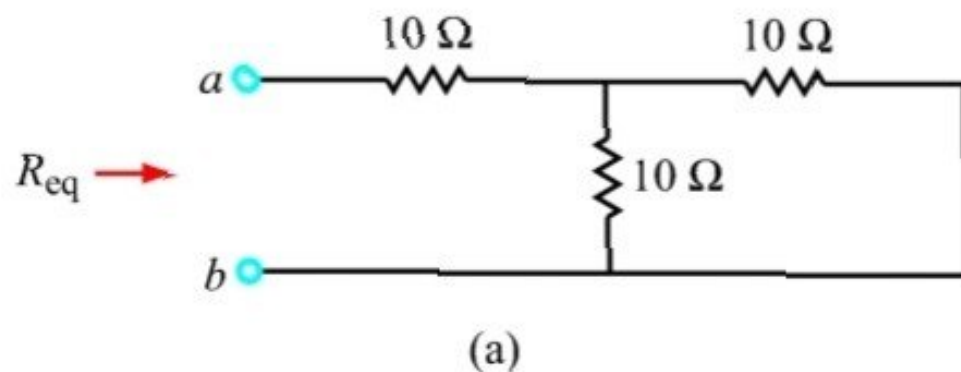

**Figure E2-9**





**Solution:**

(a)

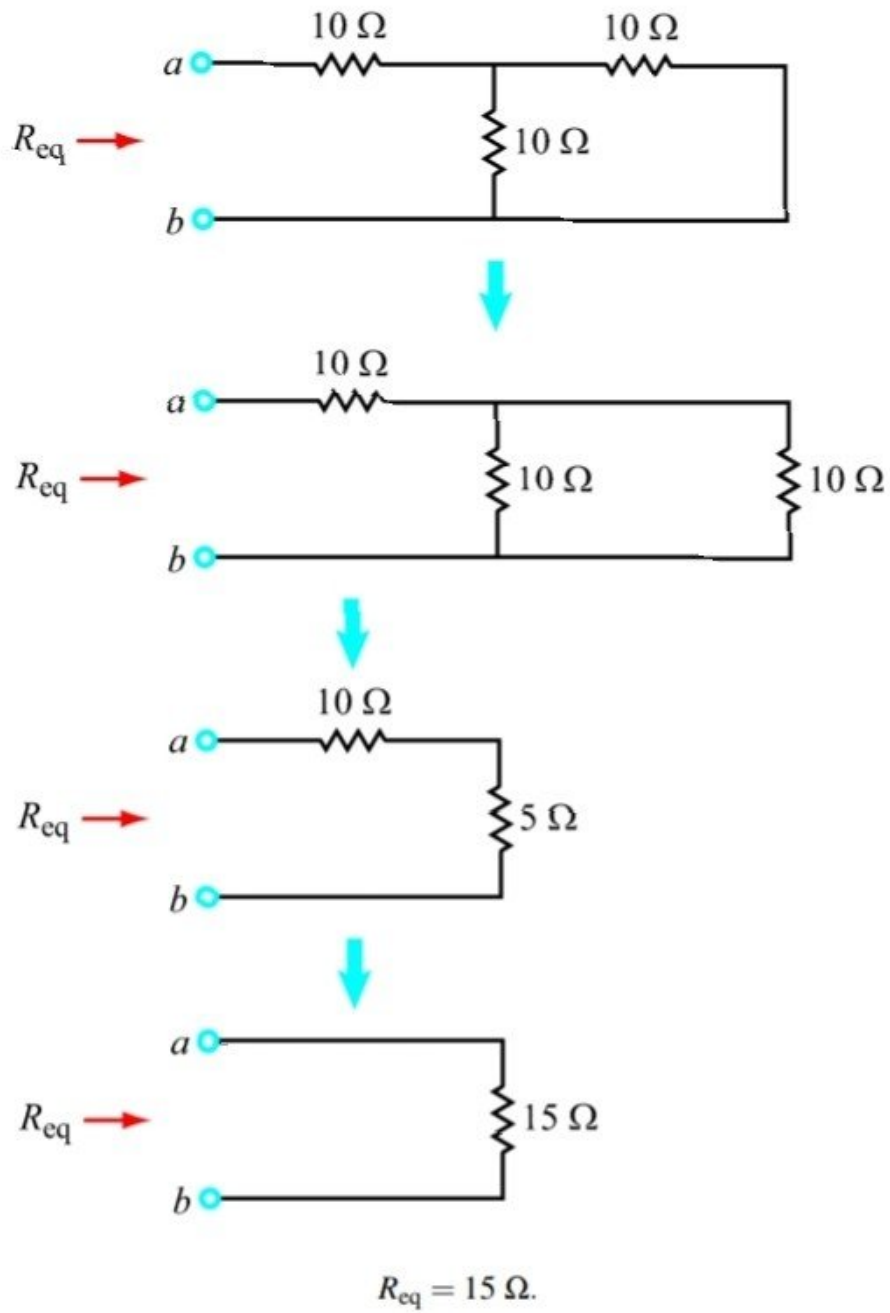


(b) Applying Y- $\Delta$  transformation



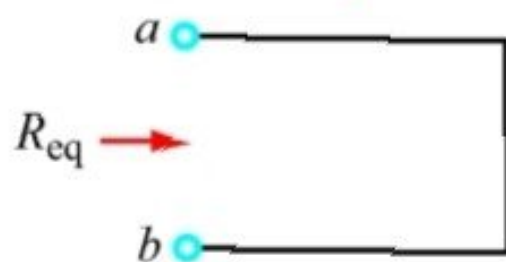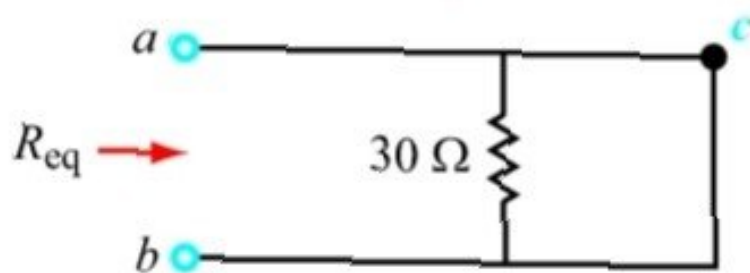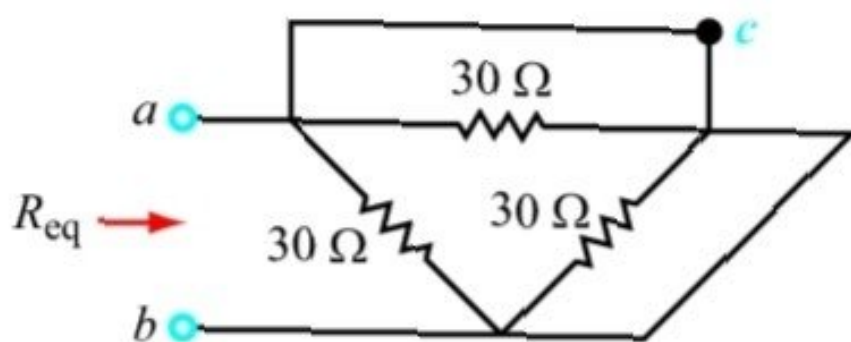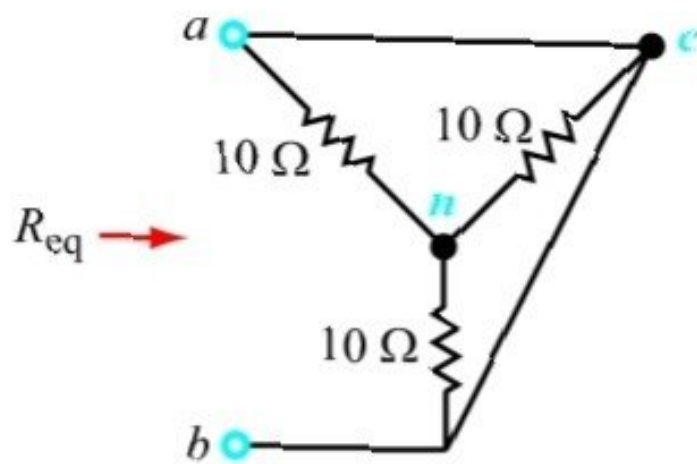

$$R_{eq} = 0.$$

**Exercise 2-11** Determine  $I$  in the two circuits of Fig. E2-11. Assume  $V_F = 0.7$  V for all diodes.

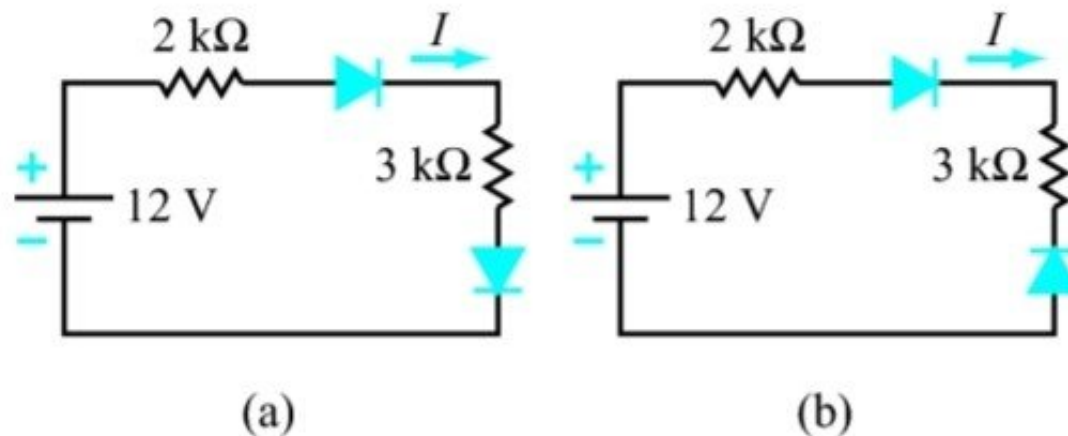

**Figure E2-11**

**Solution:**

**(a)** With  $V_F = 0.7$  V, KVL around the loop gives

$$-12 + 2 \times 10^3 I + 0.7 + 3 \times 10^3 I + 0.7 = 0,$$

which leads to

$$I = \frac{12 - 1.4}{5 \times 10^3} = 2.12 \text{ mA}.$$

**(b)** Since the diodes are biased in opposition to one another, no current can flow in the circuit. Hence

$$I = 0.$$

**Exercise 3-1** Apply nodal analysis to determine the current  $I$ .


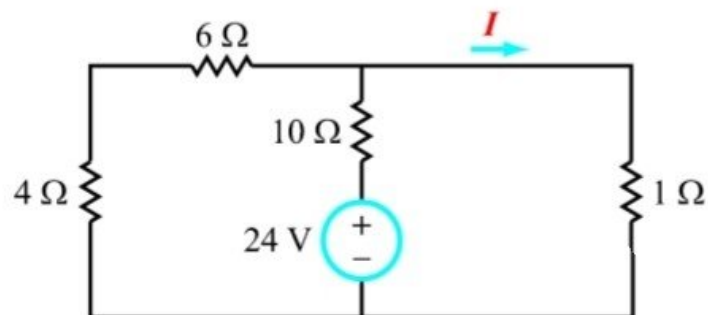


Figure E3-1

**Solution:**

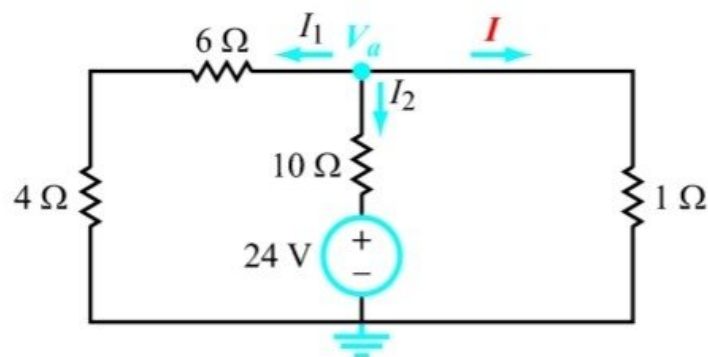

$$I_1 + I_2 + I = 0$$

$$I_1 = \frac{V_a}{10}, \quad I_2 = \frac{V_a - 24}{10}, \quad I_3 = \frac{V_a}{1}$$

Hence,

$$\begin{aligned} \frac{V_a}{10} + \frac{V_a - 24}{10} + V_a &= 0, \\ V_a \left( \frac{1}{10} + \frac{1}{10} + 1 \right) &= \frac{24}{10}, \end{aligned}$$

which leads to

$$V_a = 2 \text{ V}, \quad I = \frac{V_a}{1} = 2 \text{ A}.$$

**Exercise 3-2** Apply nodal analysis to find  $V_a$ .


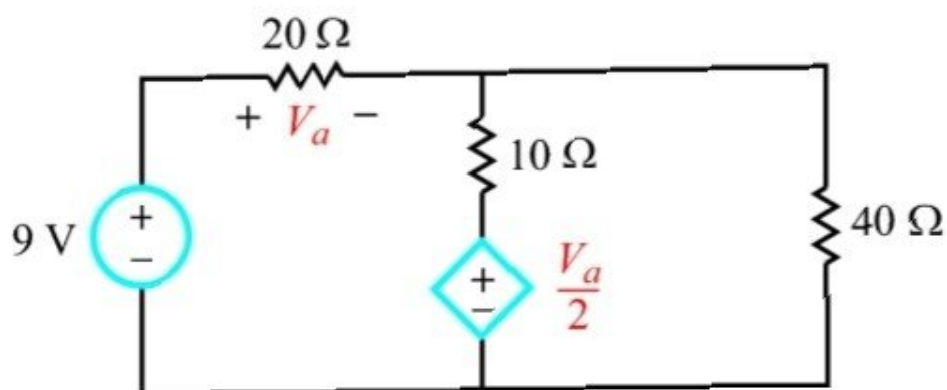


Figure E3-2

**Solution:**

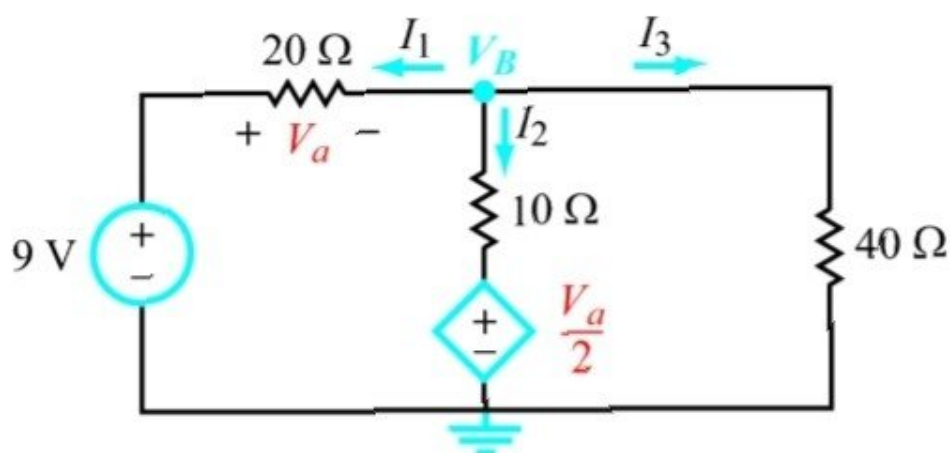

$$I_1 + I_2 + I_3 = 0$$

$$I_1 = \frac{V_B - 9}{20}, \quad I_2 = \frac{V_B - \frac{V_a}{2}}{10}, \quad I_3 = \frac{V_B}{40}.$$

Hence,


$$\frac{V_B - 9}{20} + \frac{V_B - \frac{V_a}{2}}{10} + \frac{V_B}{40} = 0.$$

Also,

$$V_a = 9 - V_B.$$


Solution gives:  $V_a = 5$  V.

**Exercise 3-4** Apply mesh analysis to determine  $I$ .

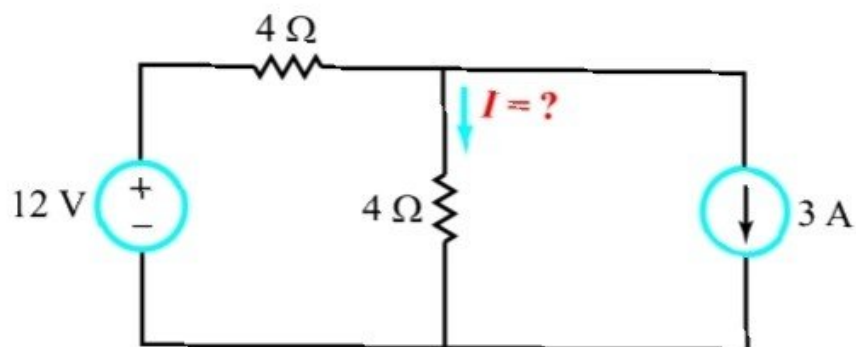

**Figure E3-4**

**Solution:**

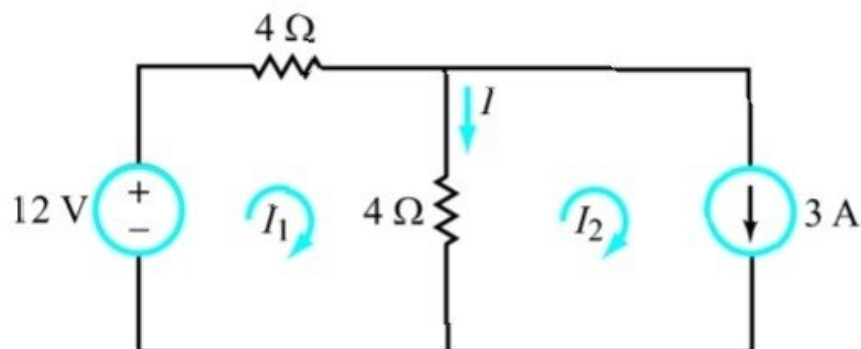

$$\text{Mesh 1: } -12 + 4I_1 + 4(I_1 - I_2) = 0$$

$$\text{Mesh 2: } I_2 = 3 \text{ A}$$


$$4I_1 + 4I_1 - 4 \times 3 = 12$$

$$8I_1 = 24$$

$$I_1 = 3 \text{ A.}$$


$$\Rightarrow I = I_1 - I_2 = 3 - 3 = 0.$$

**Exercise 3-5** Determine the current  $I$  in the circuit of Fig. E3-5.

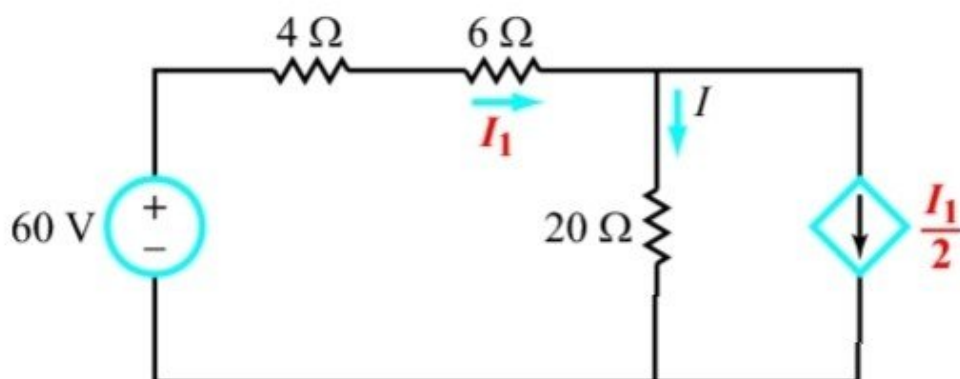

**Figure E3-5**

**Solution:**

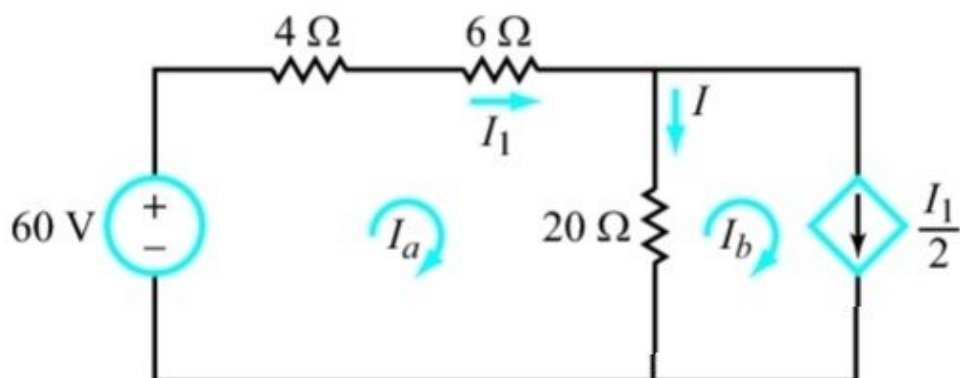

$$\text{Mesh 1: } -60 + 10I_a + 20(I_a - I_b) = 0$$

$$\text{Mesh 2: } I_b = \frac{I_1}{2}$$

Also,

$$I_1 = I_a.$$

Hence,

$$I_b = \frac{I_a}{2},$$

$$-60 + 10I_a + 20\left(I_a - \frac{I_a}{2}\right) = 0,$$

which simplifies to


$$20I_1 = 60$$

or

$$I_a = 3 \text{ A},$$


$$I = I_a - I_b = I_a - \frac{I_a}{2} = \frac{I_a}{2} = \frac{3}{2} = 1.5 \text{ A}.$$

**Exercise 3-6** Apply mesh analysis to determine  $I$  in the circuit of Fig. E3-6.

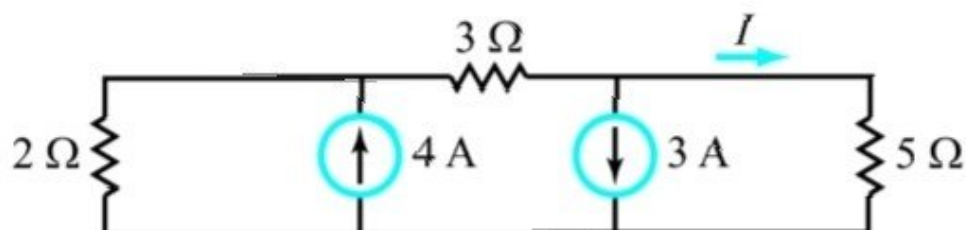

**Figure E3-6**

**Solution:**

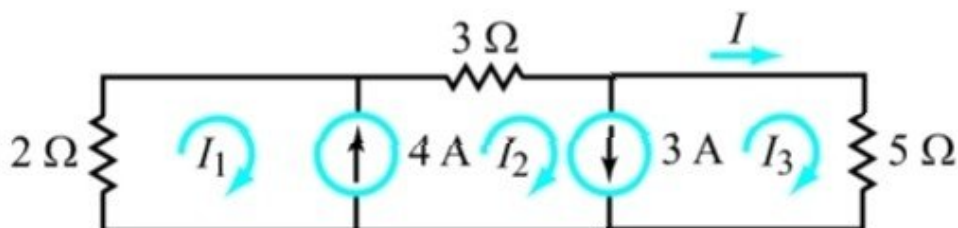

$$\text{Outside mesh: } 2I_1 + 3I_2 + 5I_3 = 0.$$

Also,

$$I_2 - I_1 = 4 \text{ A}, \quad I_2 - I_3 = 3 \text{ A}.$$

Hence,

$$I_1 = I_2 - 4 = (I_3 + 3) - 4 = I_3 - 1$$

$$I_2 = I_3 + 3$$


$$2(I_3 - 1) + 3(I_3 + 3) + 5I_3 = 0$$

$$10I_3 = 2 - 9$$

$$I_3 = -0.7 \text{ A}$$

$$I = I_3 = -0.7 \text{ A}.$$

**Exercise 3-7** Apply the node-analysis by-inspection method to generate the node voltage matrix for the circuit in Fig. E3-7.

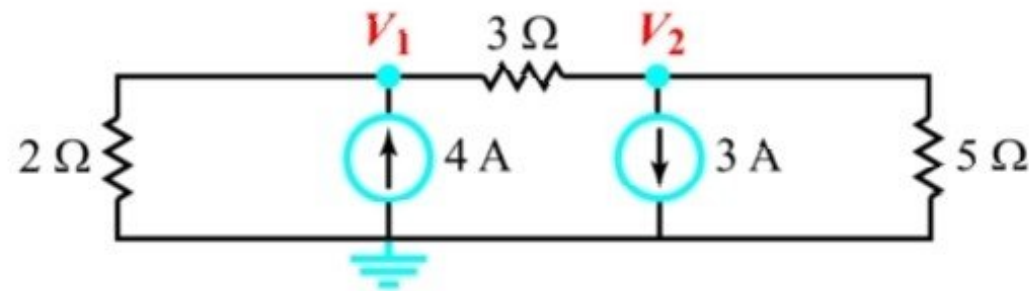

**Figure E3.7**

**Solution:**

$$G_{11} = \frac{1}{3} + \frac{1}{2} = \frac{5}{6}, \quad G_{22} = \frac{1}{3} + \frac{1}{5} = \frac{8}{15}, \quad G_{12} = -\frac{1}{3} = G_{21}, \quad G_{11} = \frac{5}{6},$$

Hence,


$$\begin{bmatrix} \frac{5}{6} & -\frac{1}{3} \\ -\frac{1}{3} & \frac{8}{15} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 4 \\ -3 \end{bmatrix}.$$

By MATLAB software,

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 3.4 \text{ V} \\ -3.5 \text{ V} \end{bmatrix}.$$



**Exercise 3-8** Use the by-inspection method to generate the mesh current matrix for the circuit in Fig. E3-8.

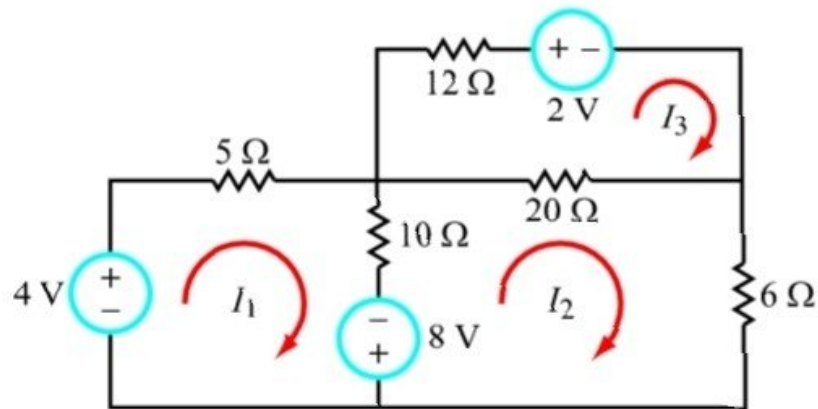

**Figure E3-8**

**Solution:**

$$R_{11} = 5 + 10 = 15$$

$$R_{22} = 10 + 20 + 6 = 36$$

$$R_{33} = 20 + 12 = 32$$

$$R_{12} = R_{21} = -10$$

$$R_{13} = R_{31} = 0$$

$$R_{23} = R_{32} = -20$$

Hence,

$$\mathbf{R} = \begin{bmatrix} 15 & -10 & 0 \\ -10 & 36 & -20 \\ 0 & -20 & 32 \end{bmatrix}$$

$$\mathbf{V} = \begin{bmatrix} 8 + 4 = 12 \\ -8 \\ -2 \end{bmatrix}$$

$$\mathbf{I} = \mathbf{R}^{-1}\mathbf{V} = \begin{bmatrix} 0.7505 \\ -0.0743 \\ -0.1089 \end{bmatrix}$$

$$\therefore I_1 = 0.75 \text{ A}$$

$$I_2 = -0.07 \text{ A}$$

$$I_3 = -0.11 \text{ A}$$

**Exercise 3-9** Apply the source-superposition method to determine the current  $I$  in the circuit of Fig. E3-9.


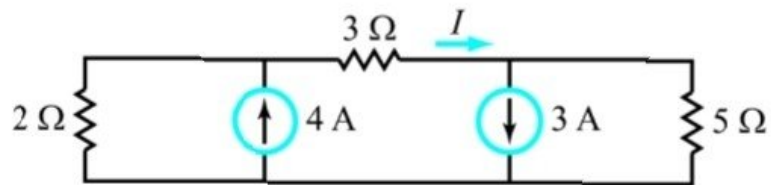
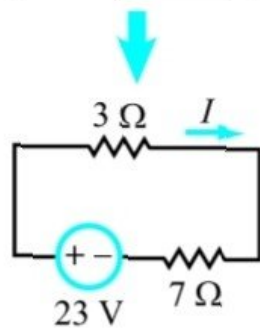
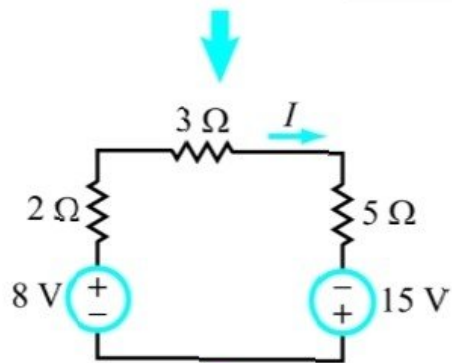



Figure E3-9

**Solution:**

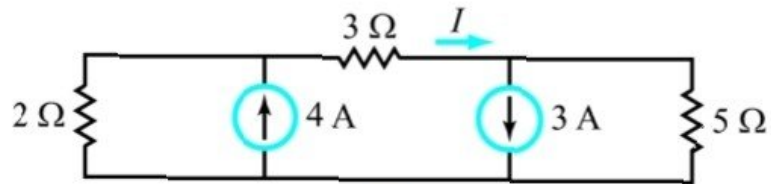




$$I = \frac{23}{3+7} = 2.3 \text{ A.}$$

**Exercise 3-10** Apply source superposition to determine  $V_{\text{out}}$  in the circuit of Fig. E3-10.

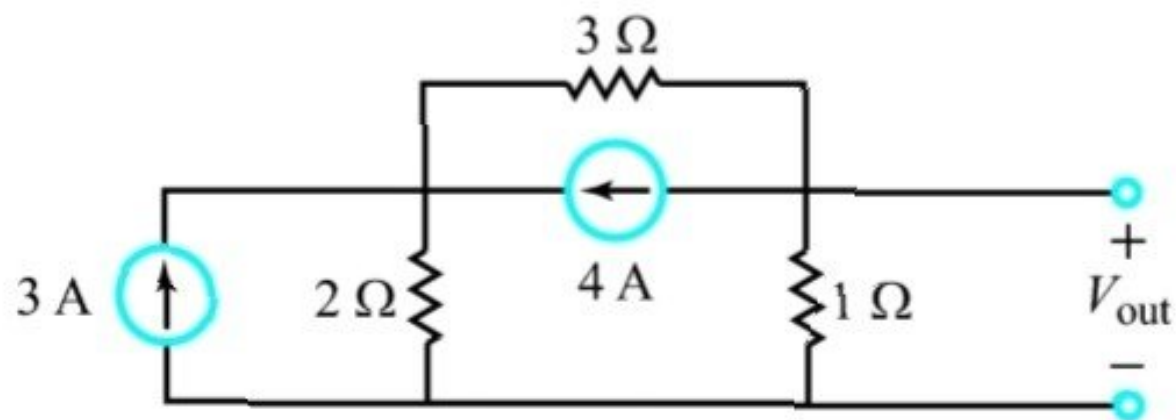

**Figure E3-10**

**Solution:**

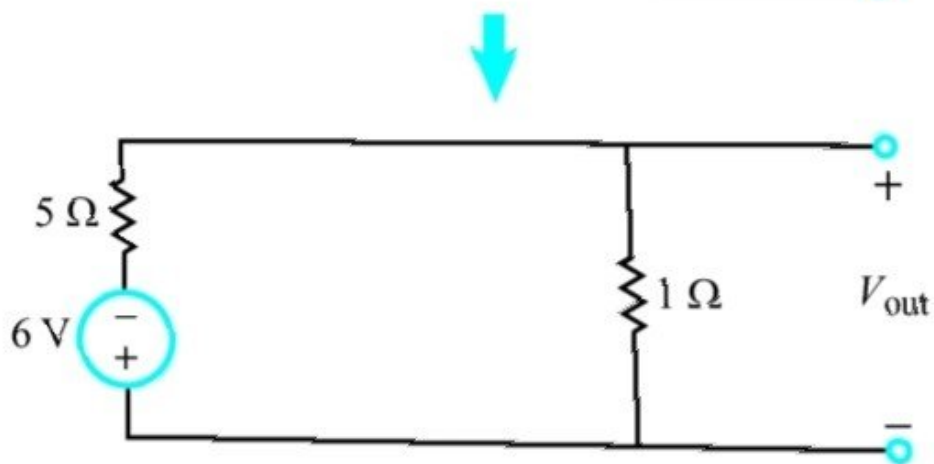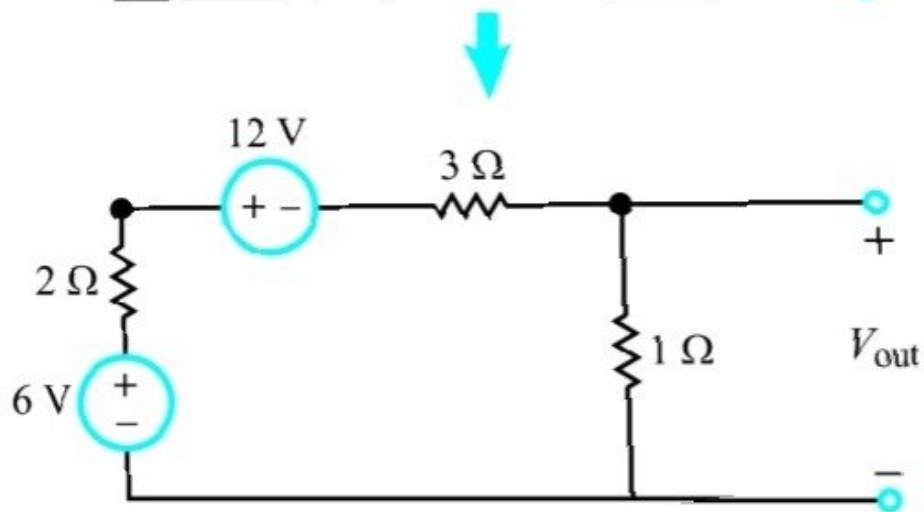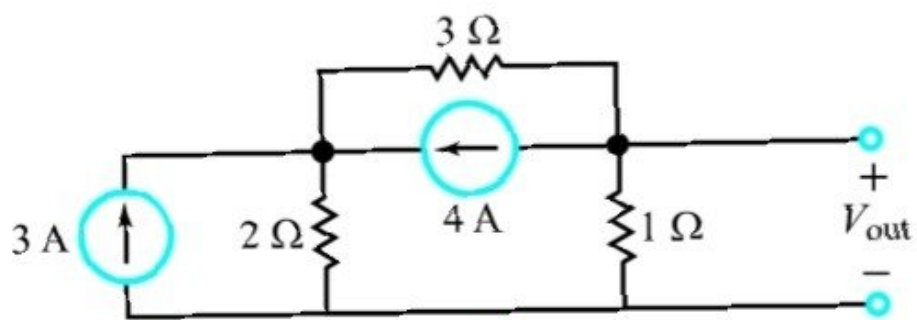

By voltage division,

$$V_{\text{out}} = \frac{-6 \times 1}{5 + 1} = -1\text{ V},$$